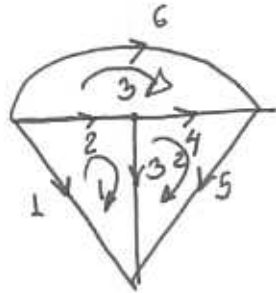


Examen

Problema 1

grafo orientado



matriz de mallos

$$M = \begin{bmatrix} -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 & 0 \\ 0 & -1 & 0 & -1 & 0 & 1 \end{bmatrix} \quad M^T = \begin{bmatrix} -1 & 0 & 0 \\ 1 & 0 & -1 \\ 1 & -1 & 0 \\ 0 & 1 & -1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

matriz impedancia de ramos

$$Z_b = \begin{bmatrix} R_1 & 0 & 0 & 0 & 0 & 0 \\ 0 & sL_1 & 0 & -sM & 0 & 0 \\ 0 & 0 & \frac{1}{sC_1} & 0 & 0 & 0 \\ 0 & -sM & 0 & sL_2 & 0 & 0 \\ 0 & 0 & 0 & 0 & R_2 & 0 \\ 0 & 0 & 0 & 0 & 0 & \frac{1}{sC_2} \end{bmatrix}$$

$$J_s = \begin{bmatrix} -I_f \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad V_s = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ \alpha i_{L_1} \\ 0 \end{bmatrix} \quad Z_b J_s - V_s = \begin{bmatrix} -R_1 I_f \\ 0 \\ 0 \\ 0 \\ -\alpha i_{L_1} \\ 0 \end{bmatrix}$$

$$Z_b M^T = \begin{bmatrix} -R_1 & 0 & 0 \\ sL_1 & -sM & -sL_1 + sM \\ \frac{1}{sC_1} & -\frac{1}{sC_1} & 0 \\ -sM & sL_2 & sM - sL_2 \\ 0 & R_2 & 0 \\ 0 & 0 & \frac{1}{sC_2} \end{bmatrix}$$

$$Z_M = \begin{bmatrix} R_1 + sL_1 + \frac{1}{sC_1} & -sM - \frac{1}{sC_1} & -sL_1 + sM \\ -sM - \frac{1}{sC_1} & \frac{1}{sC_1} + sL_2 + R_2 & sM - sL_2 \\ -sL_1 + sM & sM - sL_2 & sL_1 - sM + sL_2 + \frac{1}{sC_2} \end{bmatrix}$$

finalmente

$$M(Z_b J_s - V_s) = \begin{bmatrix} R_1 I_f \\ -\alpha i_{L_1} \\ 0 \end{bmatrix} \quad \begin{bmatrix} R_1 + sL_1 + \frac{1}{sC_1} & -sM - \frac{1}{sC_1} & sM - sL_1 \\ -sM - \frac{1}{sC_1} + \alpha & \frac{1}{sC_1} + sL_2 + R_2 & sM - sL_2 - \alpha \\ sM - sL_1 & sM - sL_2 & sL_1 + sL_2 - 2sM + \frac{1}{sC_2} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} R_1 I_f \\ 0 \\ 0 \end{bmatrix}$$

$$i_{L_1} = (I_1 - I_3)$$

Examen


Problema 2

condiciones iniciales

$$i_L(0) = \frac{12}{1/5} = 60 \text{ A}$$

$$V_C(0) = 12 \text{ V}$$

Red en Laplace para método de los mallas

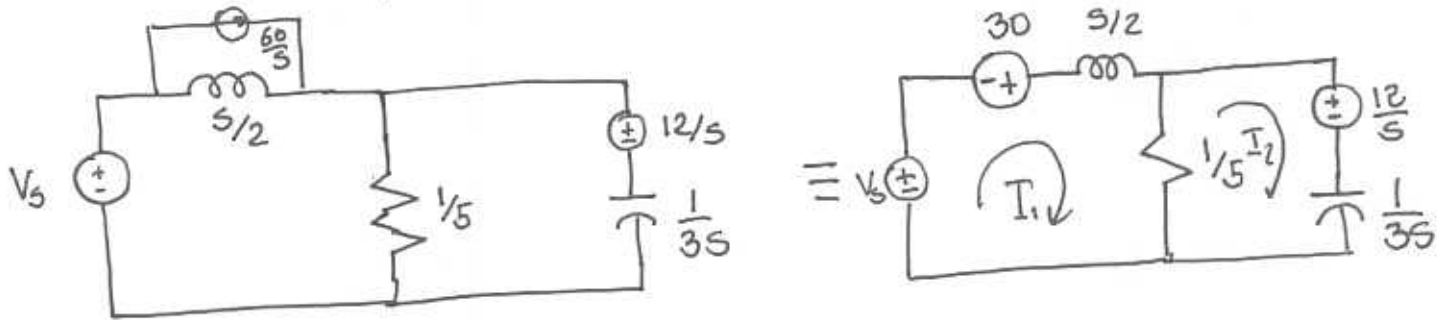

$$\begin{bmatrix} \frac{s}{2} + \frac{1}{5} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{3s} + \frac{1}{5} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_s + 30 \\ -\frac{12}{s} \end{bmatrix}$$

b) RESC

$$\begin{bmatrix} \frac{s}{2} + \frac{1}{5} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{3s} + \frac{1}{5} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix} \quad \Delta = \left(\frac{s}{2} + \frac{1}{5}\right)\left(\frac{1}{3s} + \frac{1}{5}\right) - \frac{1}{25}$$

$$\Delta = \frac{1}{6} + \frac{s}{10} + \frac{1}{15s}$$

$$\Delta_2 = V_s/5$$

$$I_2 = \frac{V_s/5}{\frac{s}{10} + \frac{1}{6} + \frac{1}{15s}} \quad \begin{matrix} / \cdot 10s \\ / \cdot 10s \end{matrix}$$

$$I_2 = \frac{2sV_s}{s^2 + \frac{5}{3}s + \frac{2}{3}}$$

$$V_C = \frac{1}{3s} I_2$$

$$V_C(s) = \frac{2/3 V_s}{s^2 + \frac{5}{3}s + \frac{2}{3}}$$

$$V_s(s) = \frac{4}{(s+2)}$$

$$V_C(s) = \frac{8/3}{(s+2)(s+1)(s+2/3)} = \frac{A}{(s+2)} + \frac{B}{(s+1)} + \frac{C}{(s+2/3)}$$

$$A = \frac{8/3}{(-2+1)(-2+2/3)} = \frac{8/3}{4/3} = 2$$

$$B = \frac{8/3}{(-1+2)(-1+2/3)} = \frac{8/3}{-1/3} = -8$$

$$C = \frac{8/3}{(-2/3+2)(-2/3+1)} = \frac{8/3}{4/9} = 6$$

$$V_c(t) = [2e^{-2t} - 8e^{-t} + 6e^{-2/3t}] u(t)$$

c) RENC

$$\begin{bmatrix} \frac{5}{2} + \frac{1}{5} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{35} + \frac{1}{5} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 30 \\ -\frac{12}{5} \end{bmatrix}$$

$$\Delta_2 = -\frac{12}{5} \left(\frac{5}{2} + \frac{1}{5} \right) + 6 = -6 - \frac{12}{55} + 6 = -\frac{12}{55}$$

$$I_2 = \frac{-\frac{12}{55}}{\frac{5}{10} + \frac{1}{6} + \frac{1}{155}} \xrightarrow{/105} I_2(s) = \frac{-24}{s^2 + \frac{5}{3}s + \frac{2}{3}}$$

$$V_c(s) = \frac{1}{35} I_2(s) + \frac{12}{5}$$

$$V_c(s) = \frac{-8}{s(s+1)(s+2/3)} = \frac{A}{(s+1)} + \frac{B}{(s+2/3)} + \frac{C}{s}$$

$$A = \frac{8}{-1 \cdot (-1/3)} = -24$$

$$B = \frac{8}{-2/3 \cdot 1/3} = +36$$

$$C = \frac{8}{1 \times 2/3} = -12$$

$$V_c(t) = (-24e^{-t} + 36e^{-2/3t} +) u(t)$$

otra forma sin cambiar de posición R con C

$$\begin{bmatrix} \frac{s}{2} + \frac{1}{3s} & -\frac{1}{3s} \\ -\frac{1}{3s} & \frac{1}{3s} + \frac{1}{5} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_s + 30 - \frac{12}{s} \\ \frac{12}{s} \end{bmatrix}$$

b) RESC

$$\begin{bmatrix} \frac{s}{2} + \frac{1}{3s} & -\frac{1}{3s} \\ -\frac{1}{3s} & \frac{1}{3s} + \frac{1}{5} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix} \quad \Delta = \left(\frac{s}{2} + \frac{1}{3s}\right)\left(\frac{1}{3s} + \frac{1}{5}\right) - \frac{1}{9s^2}$$

$$\Delta = \frac{s}{10} + \frac{1}{6} + \frac{1}{15s}$$

$$\Delta_2 = \frac{1}{3s} V_s \quad I_2 = \frac{\Delta_2}{\Delta} = \frac{\frac{1}{3s} V_s}{\frac{s}{10} + \frac{1}{6} + \frac{1}{15s}} \quad / \cdot 10s$$

$$I_2(s) = \frac{\frac{10}{3} V_s}{s^2 + \frac{5}{3}s + \frac{2}{3}} = \frac{\frac{40}{3}}{(s+2)(s+1)(s+2/3)} \quad V_R = V_C = \frac{1}{5} I_2(s)$$

$$\Rightarrow V_C(s) = \frac{8/3}{(s+2)(s+1)(s+2/3)} \quad \Rightarrow V_C(t) = [2e^{-2t} - 8e^{-t} + 6e^{-2/3t}] u(t)$$

c) RENC

$$\Delta_2 = \left(\frac{s}{2} + \frac{1}{3s}\right) \cdot \frac{12}{s} + \frac{1}{3s} \left(30 - \frac{12}{s}\right) = 6 + \frac{4}{s^2} + \frac{10}{s} - \frac{4}{s^2}$$

$$\Delta_2 = 6 + \frac{10}{s}$$

$$I_2 = \frac{6 + 10/s}{\frac{s}{10} + \frac{1}{6} + \frac{1}{15s}} \quad / \cdot 10s \quad \Rightarrow I_2 = \frac{60s + 100}{s^2 + \frac{5}{3}s + \frac{2}{3}} \quad V_R = V_C = \frac{1}{5} I_2(s)$$

$$V_C(s) = \frac{12s + 20}{(s+1)(s+2/3)} = \frac{A}{(s+1)} + \frac{B}{(s+2/3)}$$

$$A = \frac{-12 + 20}{-1/3} = -24$$

$$B = \frac{-8 + 20}{1/3} = 36$$

$$V_C(t) = (-24e^{-t} + 36e^{-2/3t}) u(t)$$