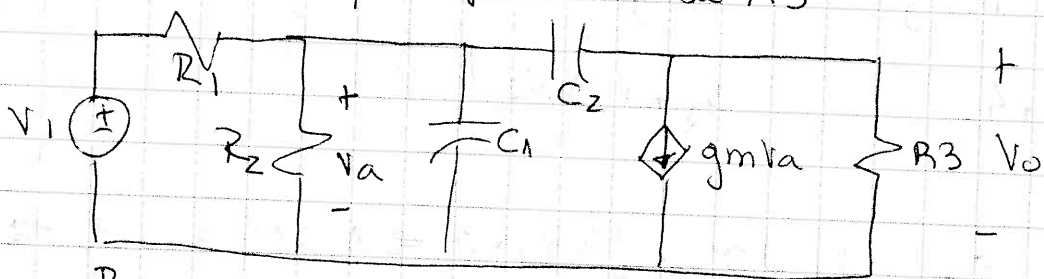


Para la red de la figura, que es lineal en variante, determine v_o y la potencia de R_3



$$R_1 = 0,1 \, \Omega$$

$$R_2 = 0,5 \, \Omega$$

$$R_3 = 1 \, \Omega$$


$$C_1 = 100 \, \text{F}$$

$$C_2 = 3 \, \text{F}$$

$$g_m = 40 \, \text{A/V}$$

$$v_1 = \cos(t)$$

Solución:

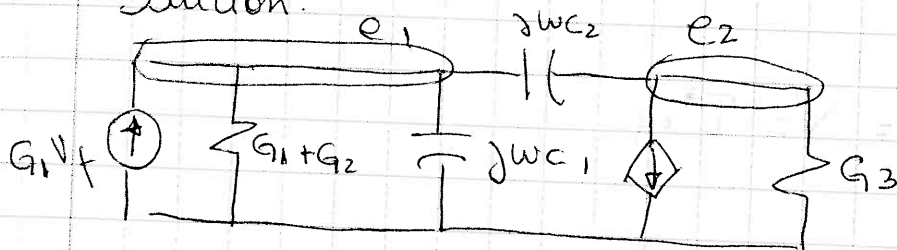

$$\begin{bmatrix} G_1 + G_2 + j\omega(C_1 + C_2) & -j\omega C_2 \\ -j\omega C_2 & j\omega C_2 + G_3 \end{bmatrix} \begin{pmatrix} e_1 \\ e_2 \end{pmatrix} = \begin{pmatrix} G_1 v_f \\ -g_m v_a \end{pmatrix}$$

Tenemos que $v_a = e_1 \Rightarrow -g_m v_a = g_m e_1$
 $\Rightarrow$ introduzco en la matriz.

$$\begin{bmatrix} G_1 + G_2 + j\omega(C_1 + C_2) & -j\omega C_2 \\ -j\omega C_2 + g_m & G_3 + j\omega C_2 \end{bmatrix} \begin{pmatrix} e_1 \\ e_2 \end{pmatrix} = \begin{pmatrix} G_1 v_f \\ 0 \end{pmatrix}$$

Dando valores

$$\begin{bmatrix} 12 + 103j & -3j \\ -3j + 40 & 3j + 1 \end{bmatrix} \begin{pmatrix} e_1 \\ e_2 \end{pmatrix} = \begin{pmatrix} 10 \\ 0 \end{pmatrix}$$

$$\Rightarrow e_2 = 1,0356 \angle 37,63^\circ \Rightarrow$$

$$v_o = 1,0356 \cos(t + 9,65)$$

$$P = \frac{V^2}{2R_3} = 0,335 \text{ W}$$

Recuerden!!

$$P = \frac{V I^*}{2} = V_{ef} I_{ef}^*$$

$$P = \frac{V(V^*)}{2(\bar{Z})}$$

$$P = \frac{|V|^2}{2Z^*} = \frac{|V_{ef}|^2}{Z^*}$$