

P4

①

$$V = \frac{1}{\sqrt{\epsilon_r \epsilon_0 \mu_0}}$$

$$\mu_0 = 1,2566 \times 10^{-6}$$

$$\epsilon_0 = 8,8541 \times 10^{-12}$$

$$L_{1,2} \Rightarrow \epsilon_r = 4 \quad y \quad L_3 \Rightarrow \epsilon_r = 9$$

$$L_1 = 0,2125 \text{ m}$$

$$L_2 = 0,15 \text{ m}$$

$$L_3 = 0,15 \text{ m}$$

REEMPLAZANDO

$$V_{1,2} = 1,499 \times 10^8$$

$$V_2 = 9,9933 \times 10^7$$

$$y \quad V = \frac{2\pi b}{\beta} \quad \text{con } b = 16 \text{ Hz}$$

CONSTANTES DE PROPAGACIÓN $\gamma = \alpha + j\beta$
 COMO LAS LINEAS NO TIENEN PERDIDAS
 $\alpha_1 = \alpha_2 = \alpha_3 = 0$

Reemplazando

$$\beta_1 = \frac{2\pi \cdot 16 \text{ Hz}}{1,499 \times 10^8} = 41,9158 \quad y \quad \beta_1 = \beta_2 \Rightarrow \beta_2 = 41,9158 \left[\frac{\text{rad}}{\text{m}} \right]$$

$$\beta_3 = \frac{2\pi \cdot 16 \text{ Hz}}{9,9933 \times 10^7} = 62,874 \left[\frac{\text{rad}}{\text{m}} \right]$$


$$\Rightarrow \gamma_{1,2} = j 41,9158 \quad y \quad \gamma_3 = j 62,874$$

$$\text{con } Z_{01} = 50 \Omega \quad y \quad Z_L = 75 - j150 \Omega$$

$$Z_{L2} = Z_{01} \left[\frac{Z_L + j Z_{01} \tan(\beta_2 \cdot 0,15)}{Z_{01} + j Z_L \tan(\beta_2 \cdot 0,15)} \right] = 12,6608 + j50,0953j$$

②
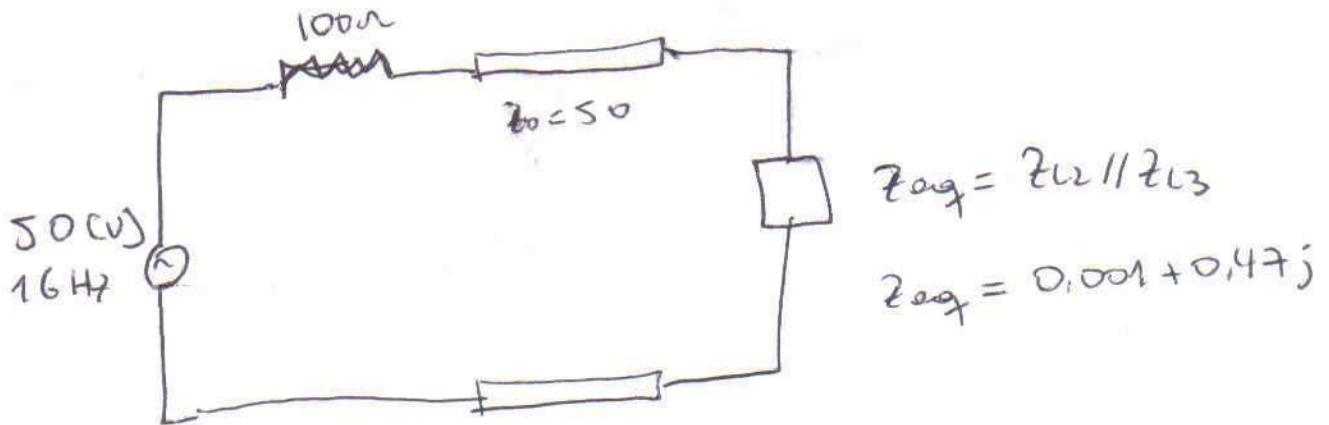
$$Z_{L3} = j Z_{02} \tan(\beta_3 \cdot 0,15) = 0,4742j$$



$$P_1 = \frac{Z_{eq} - 50}{Z_{eq} + 50} = -0,9998 + 0,0188j$$

$$P_1 = -0,9998 + 0,0188j$$

$$V^- = V^+ P_1 \quad \text{con} \quad V^+ = \frac{50 \cdot 50}{50 + 100} = 16,667 \text{ [V]}$$

$$\Rightarrow V^- = -16,6633 + 0,3133j$$

$$ROE = \frac{V_{MAX}}{V_{MIN}} \quad \text{ou} \quad ROE = \frac{1 + |P_1|}{1 - |P_1|}$$

$$\Rightarrow ROE = 4,7731 \times 10^4$$

$$Z_{INPUT} = Z_0 \left[\frac{Z_{eq} + j Z_0 \tan(\beta_1 \cdot 0,2125)}{Z_0 + j Z_{eq} \tan(\beta_1 \cdot 0,2125)} \right] = 0,0014 - 27,8545j$$

$$V_{EL} = \frac{50 \cdot Z_{INPUT}}{Z_{INPUT} + 100} = 3,6066 - 12,9241j \Rightarrow P_{2L} = \frac{1}{2} \operatorname{Re} \left(\frac{V_{EL}^2}{Z_{INPUT}^*} \right)$$

LIPEAS SIN
PERDIDAS

$$P_{2L} = 1,624 \times 10^{-4}$$