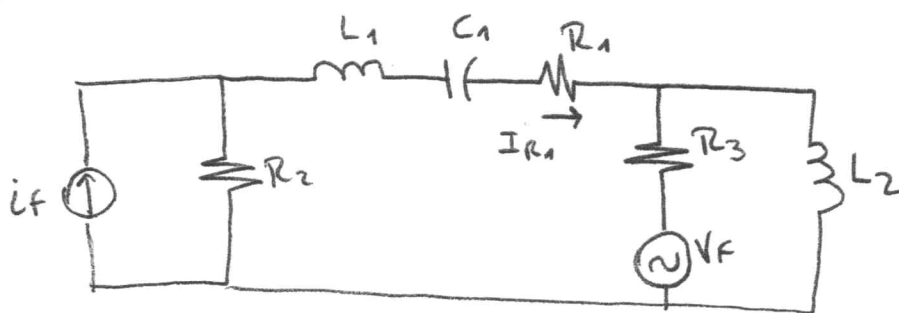


P1 | Aplicando el método de circuitos regionales, obtener el valor de I_{R_1} .




- $R_1 = 10 [\Omega]$
- $R_2 = 20 [\Omega]$
- $R_3 = 5 [\Omega]$
- $L_1 = 1 [H]$
- $L_2 = 1 [H]$
- $C_1 = 0,2 [F]$

$$v_f = 100 \sin(10t + 30^\circ) \Rightarrow \dot{v}_f = 100 \angle 30^\circ - 90^\circ \Rightarrow \boxed{\dot{v}_f = 100 \angle -60^\circ}$$

$$i_f = 200 \cos(20t + 45^\circ) \Rightarrow \boxed{\dot{i}_f = 200 \angle 45^\circ}$$

SOL | Método Regional $\Rightarrow$ Impedancias $\hat{z}$

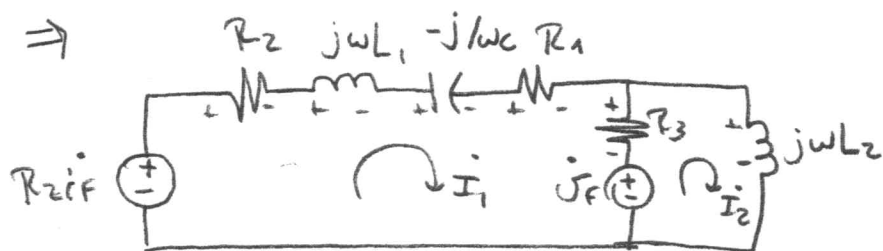

$$\Rightarrow (R_2 + j\omega L_1 - j/\omega c + R_1)I_1 + R_3(I_1 - I_2) + U_F = R_2 i_F$$

$$\Rightarrow (R_1 + R_2 + R_3 + j\omega L_1 - j/\omega c)I_1 + (-R_3)I_2 = R_2 i_F - U_F$$

$$-R_3(I_1 - I_2) + j\omega L_2 \cdot I_2 = U_F$$

$$\Rightarrow I_1(-R_3) + I_2(R_3 + j\omega L_2) = U_F$$

$$\Rightarrow \begin{bmatrix} R_1 + R_2 + R_3 + j\omega L_1 - j/\omega c & -R_3 \\ -R_3 & j\omega L_2 + R_3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} R_2 i_F - U_F \\ U_F \end{bmatrix}$$

Ahora, aplico principio de superposición (por tener las fuentes $\neq \omega$'s)

$\Rightarrow$ 1er caso $U_F = 0$ y obtengo I_1

$\Rightarrow$ 2do caso $i_F = 0$ y obtengo I_2

i) $U_F = 0 \Rightarrow \omega = 20$ (ω de i_F)

$$\Rightarrow \begin{bmatrix} 35 + 19.75j & -5 \\ -5 & 20j + 5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 4000 \angle 45^\circ \\ 0 \end{bmatrix}$$

$$I_1 = \frac{\Delta_1}{\Delta} \quad \Delta = (35 + 19.75j)(20j + 5) - 25 = -245 + j798.75 = 835.48 \angle 107.05^\circ \text{ (T.I.)}$$

$$\Delta_1 = (4000 \angle 45^\circ)(20j + 5) = 82462.1 \angle 120^\circ$$

$$\Rightarrow I_1 = \frac{82462.1 \angle 120^\circ}{835.48 \angle 107.05^\circ} \Rightarrow I_1 = 98.7 \angle 12.95^\circ$$

$$\boxed{\text{ii}} \quad \dot{v}_F = 0 \Rightarrow \omega = 10 (\omega \text{ de VF})$$

$$\Rightarrow \begin{bmatrix} 35 + 9,5j & -5 \\ -5 & 10j + 5 \end{bmatrix} \begin{bmatrix} \dot{I}_1 \\ \dot{I}_2 \end{bmatrix} = \begin{bmatrix} -100 \angle -60^\circ \\ 100 \angle -60^\circ \end{bmatrix}$$

$$\dot{I}_1 = \frac{\Delta_1}{\Delta} \quad \Delta = (35 + 9,5j)(10j + 5) - 25 = 401,287 \angle 82,12^\circ$$

$$\Rightarrow \Delta_1 = (-100 \angle -60^\circ)(10j + 5) - (100 \angle -60^\circ) \cdot (-5) = 1000 \angle -150^\circ$$

$$\Rightarrow \dot{I}_1 = \frac{1000 \angle -150^\circ}{401,287 \angle 82,12^\circ}$$


$$\Rightarrow \dot{I}_1 = 2,49 \angle 127,87^\circ$$

("notación", en la práctica no se pueden sumar fasores de $\neq \omega$.)

$$\Rightarrow \text{Por superposición, } \Rightarrow \dot{I}_1 = \underbrace{98,7 \angle 12,95^\circ}_{(\omega = 20)} + \underbrace{2,49 \angle 127,87^\circ}_{(\omega = 10)}$$

$$\Rightarrow \boxed{I = 98,7 \cos(20t + 12,95^\circ) + 2,49 \cos(10t + 127,87^\circ)}$$

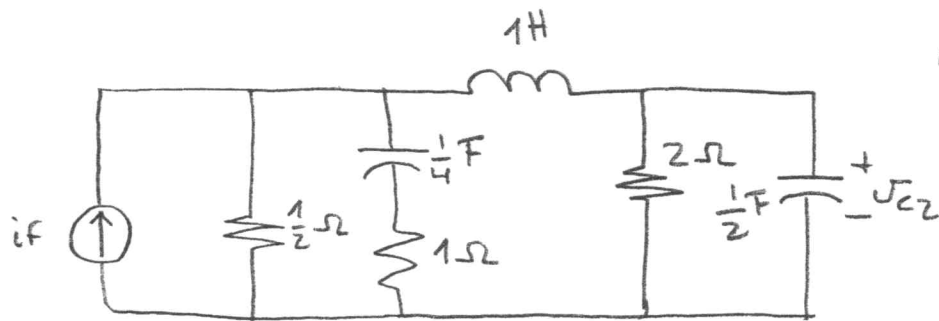
P1) Para la Red de la figura en RPS, usando el método de las mallas, determinar $v_{c2}(t)$ en RPS.



$$i_f(t) = 2 \cos(2t + \pi/4)$$

SOL $i_f = 2 \angle \pi/4 \Rightarrow i_f = 2 \angle 45^\circ$ ($\omega = 2$)

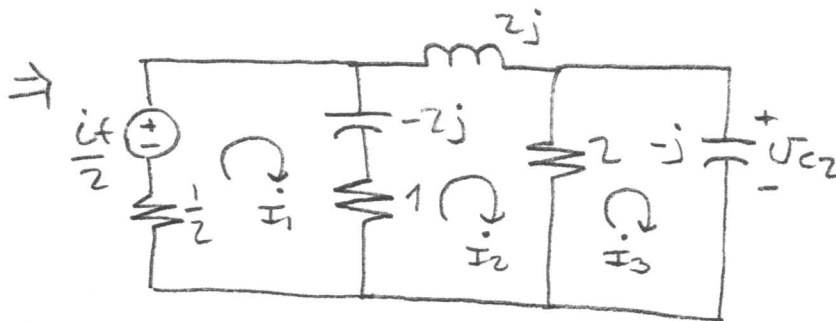Hago T.N. con i_f y método mallas $\Rightarrow$ Expresar todo como impedancias "Z".



$$Z_L = \frac{V_L}{I_L} = \frac{j\omega L I_L}{I_L} = j\omega L = 2j$$

$$Z_C = \frac{V_C}{I_C} = \frac{V_C}{j\omega C} = \frac{-j}{\omega C} = -2j$$

$$\textcircled{1} \quad \frac{1}{2}i_1 - \frac{i_f}{2} - 2j(i_1 - i_2) + (i_1 - i_2) = 0 \Rightarrow i_1 \left(\frac{3}{2} - 2j \right) + i_2(-1 + 2j) = \frac{i_f}{2}$$

$$\textcircled{2} \quad -(i_1 - i_2) - (-2j)(i_1 - i_2) + 2ji_2 + 2(i_2 - i_3) = 0$$

$$\Rightarrow i_1(-1 + 2j) + i_2(3 - 2j + 2j) + i_3(-2) = 0$$

$$\textcircled{3} \quad -2(i_2 - i_3) - j(i_3) = 0 \Rightarrow i_2(-2) + i_3(2 - j) = 0$$

$$\Rightarrow \begin{bmatrix} 3/2 - 2j & -1 + 2j & 0 \\ -1 + 2j & 3 & -2 \\ 0 & -2 & 2 - j \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} i_f/2 \\ 0 \\ 0 \end{bmatrix}$$

$\Rightarrow$ Para v_{c2} usar i_3
 $v_{c2} = i_{c2} \cdot Z_{c2}$
 $= i_3 \cdot Z_{c2}$

$$v_{c2} = i_3 \cdot (-j) \quad (*)$$

$$\Delta_3 = \begin{vmatrix} 3/2 - 2j & -1 + 2j & i_f/2 \\ -1 + 2j & 3 & 0 \\ 0 & -2 & 0 \end{vmatrix} = \frac{i_f}{2} \cdot [(-1 + 2j)(-2)] = \frac{i_f}{2} (2 - 4j)$$

$$i_f = 2 \angle 45^\circ = \sqrt{2} + j\sqrt{2} \Rightarrow \Delta_3 = (\sqrt{2} + j\sqrt{2})(1 - 2j) \Rightarrow \Delta_3 = 3\sqrt{2} - j\sqrt{2}$$

$$\Delta = \left(\frac{3}{2} - 2j\right) [3(2-j) - 4] - (-1+2j)(-1+2j)(2-j)$$

$$\Rightarrow \Delta = 7 - \frac{7}{2}j$$

$$\Rightarrow \dot{I}_3 = \frac{\Delta_3}{\Delta} = \frac{3\sqrt{2} - j\sqrt{2}}{7 - \frac{7}{2}j} \Rightarrow \dot{I}_3 = \frac{2\sqrt{2}}{5} - j \frac{2\sqrt{2}}{35} \Rightarrow \boxed{\dot{I}_3 = 0,5714 \angle 8,13^\circ}$$


$$\Rightarrow \text{Por (*)}: V_{C2} = \dot{I}_3 \cdot (-j) = (0,5714 \angle 8,13^\circ)(-j)$$

$$\Rightarrow \boxed{V_{C2} = 0,5714 \angle -81,87^\circ}$$

$$\Rightarrow \boxed{V_{C2}(t) = 0,5714 \cos(2t - 81,87^\circ)} //$$

P2 Para la Red en RPS: **a)** impedancias y admitancias de entrada, vistas desde los terminales de la fuente. **b)** Voltaje en los terminales de la fuente. **c)** Obtenga $\dot{V}_{R1}, \dot{I}_{R2}, \dot{I}_C, \dot{I}_{R1}, \dot{V}_C, \dot{V}_{R2}$

$$(i_F = 2 \cos(2t + \pi/6))$$


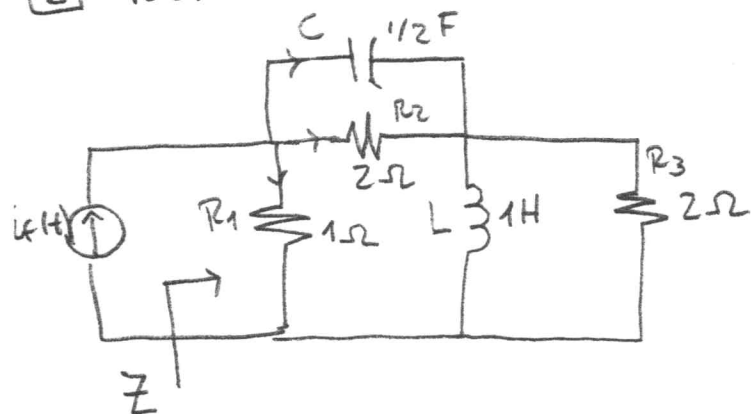


SOL **a)** Paso todo a Admitancias. $Y_L = \frac{I_L}{V_L} = \frac{I_L}{j\omega L I_L} = \frac{-j}{\omega L}$

en serie, $\frac{1}{Y_T} = \frac{1}{Y_1} + \frac{1}{Y_2} + \dots$

$Y_C = \frac{I_C}{V_C} = \frac{j\omega C V_C}{V_C} = j\omega C$


en Paralelo, $Y_T = Y_1 + Y_2 + \dots$

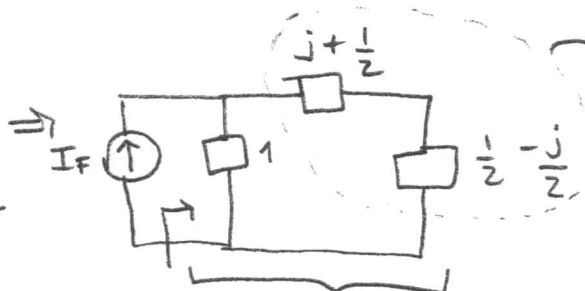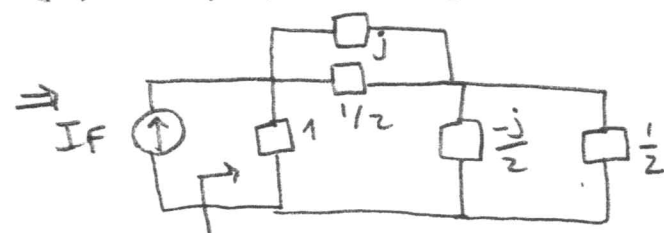

$$Y_T = \frac{(j + \frac{1}{2})(\frac{1}{2} - \frac{j}{2})}{j + \frac{1}{2} + \frac{1}{2} - \frac{j}{2}}$$

$$Y_T = \frac{7}{10} - j/10$$
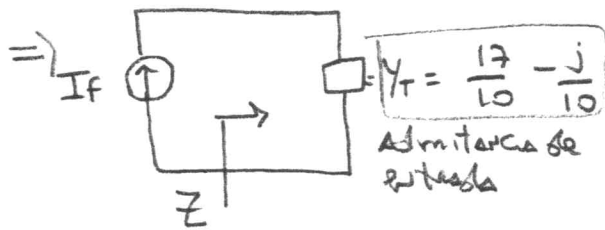
$$\Rightarrow Y_T = 1 + \frac{7}{10} - j/10 = \frac{17}{10} - j/10$$



$$\Rightarrow Z_T = \frac{1}{Y_T} \quad Z_T = \frac{1}{\frac{17}{10} - \frac{j}{10}}$$

$$\Rightarrow Z_T = \frac{17}{29} + \frac{1}{29}j$$

Impedancia de entrada.

$$\textcircled{b} \quad \dot{V}_f = Z_T \cdot \dot{I}_f$$

$$\dot{I}_f = 2 \angle \pi/6 = 2 \angle 30^\circ \quad \text{T.I.}$$

$$\Rightarrow \dot{V}_f = \left(\frac{17+j}{29} \right) \cdot (2 \angle 30^\circ) \Rightarrow \boxed{\dot{V}_f = 1,174 \angle 33,36^\circ}$$

$\Rightarrow$ el voltaje en los terminales de la fuente es:

$$\boxed{v_f(t) = 1,174 \cos(2t + 33,36^\circ)}$$

$$\textcircled{c} \quad v_{R1} = v_f \Rightarrow \boxed{v_{R1} = 1,174 \angle 33,36^\circ}$$

Además, $v_{R1} = Z_{R1} \cdot i_{R1} \Rightarrow i_{R1} = \frac{v_{R1}}{Z_{R1}} = \frac{1}{1,174 \angle 33,36^\circ}$

$$\Rightarrow \boxed{i_{R1} = 0,8517 \angle -33,36^\circ}$$

$\dot{i}_f = \dot{i}_{R1} + \dot{i}_{R2} + \dot{i}_c \quad (1) \quad \text{pero } \dot{v}_c = \dot{v}_{R2} \Rightarrow Z_c \dot{i}_c = Z_{R2} \dot{i}_{R2}$
 $\dot{i}_c = \frac{Z_{R2}}{Z_c} \dot{i}_{R2}$

$$\Rightarrow \dot{i}_c = \frac{2}{-j} \dot{i}_{R2}$$

$$\Rightarrow (1): \dot{i}_{R2} + \frac{2}{j} \dot{i}_{R2} = \dot{i}_f - \dot{i}_{R1} \quad \dot{i}_{R2} \left(1 + \frac{2}{j} \right) = \dot{i}_f - \dot{i}_{R1}$$

$$\Rightarrow \dot{i}_{R2} = \frac{(2 \angle 30^\circ) - (0,8517 \angle -33,36^\circ)}{(1 + 2/j)} \Rightarrow \boxed{\dot{i}_{R2} = 0,799 \angle 118,63^\circ}$$

$$\Rightarrow \boxed{\dot{i}_c = 1,599 \angle -151,369^\circ}$$

$$\dot{v}_c = Z_c \cdot \dot{i}_c = (-j)(1,599 \angle -151,369^\circ) \Rightarrow \boxed{\dot{v}_c = 1,599 \angle 118,631^\circ} \quad \text{y } \dot{v}_c = \dot{v}_{R2}$$

$$\Rightarrow \boxed{v_{R2} = 1,599 \angle 118,631^\circ}$$