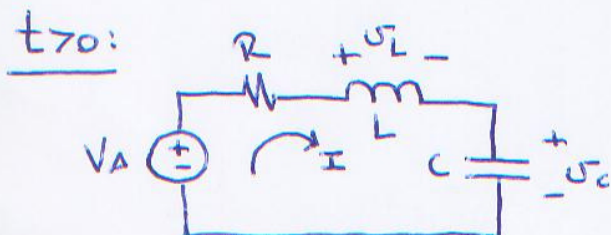


P2/C2/EL3001
2009/102
Heinz Gerdin H.

$t \text{ grande} \Rightarrow I_2 = 0 \Rightarrow V_{R2} = 0 \Rightarrow V_C = 0$

$i_L(0) = 0$
 $v_C(0) = 0$ (condiciones iniciales)



$R = R_1 + R_2$
 $I = i_L = i_C$

$\Rightarrow i_L = C \frac{dv_C}{dt}$

$\Rightarrow \frac{dv_C(0)}{dt} = i_L(0) = 0$

LVR: $V_A = V_R + v_L + v_C$

$V_A = RC \frac{dv_C}{dt} + LC \frac{d^2v_C}{dt^2} + v_C \Rightarrow \frac{d^2v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{v_C}{LC} = \frac{V_A}{LC}$

$v_C(t) = v_{Cp}(t) + v_{Ch}(t)$

$v_{Cp}(t)$: $\frac{v_C}{LC} = \frac{V_A}{LC} \Rightarrow v_{Cp}(t) = V_A$

$v_{Ch}(t)$: $\frac{d^2v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{v_C}{LC} = 0 \Rightarrow s_{1,2} = \frac{-R}{2L} \pm \frac{1}{2} \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}$

Reemplazando valores: $s_{1,2} = -2500 \pm 500\sqrt{7} \Rightarrow \text{Respuesta sobreamortiguada.}$

$v_C(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t} + V_A$ ($t > 0$)
¿ K_1, K_2 ?

$v_C(0) = 0 = K_1 + K_2 + V_A$
 $\frac{dv_C(0)}{dt} = 0 = s_1 K_1 + s_2 K_2$

$\Rightarrow v_C(t) = \left\{ \frac{s_2 V_A}{s_1 - s_2} e^{s_1 t} - \frac{s_1 V_A}{s_1 - s_2} e^{s_2 t} + V_A \right\} u(t)$ (reemplazando valores...)

$\Rightarrow v_C(t) = \left\{ -11,063 e^{-438,45t} + 1,063 e^{-4561,56t} + 10 \right\} u(t)$

b i. $V_{out} = V_{C2}$ (1)

• $V_{in} = R_1 \cdot i_{C1} + V_{C1} + V_{out}$ (2) $i_{C1} = C_1 \frac{\partial V_{C1}}{\partial t}$

• $V_{C1} = R_2 C_2 \frac{\partial V_{C2}}{\partial t}$ (3)

(3) en (2) $\Rightarrow V_{in} = R_1 C_1 R_2 C_2 \frac{\partial^2 V_{C2}}{\partial t^2} + R_2 C_2 \frac{\partial V_{C2}}{\partial t} + V_{out}$

y usando (1) y reordenando términos:

$$\frac{\partial^2 V_{out}}{\partial t^2} + \frac{1}{R_1 C_1} \frac{\partial V_{out}}{\partial t} + \frac{V_{out}}{R_1 C_1 R_2 C_2} = \frac{V_{in}}{R_1 C_1 R_2 C_2} //$$

ii de la RENC:

$$S_{1,2} = \frac{-1}{2R_1 C_1} \pm \frac{1}{2} \sqrt{\underbrace{\frac{1}{R_2^2 C_2^2} - \frac{4}{R_1 C_1 R_2 C_2}}_{\Delta}}$$

y analizando Δ , se ve que:

$R_2 C_2 > 4 R_1 C_1 \Rightarrow$ Respuesta sobreamortiguada

$R_2 C_2 = 4 R_1 C_1 \Rightarrow$ Respuesta críticamente amortiguada

$R_2 C_2 < 4 R_1 C_1 \Rightarrow$ Respuesta infraamortiguada.

//