

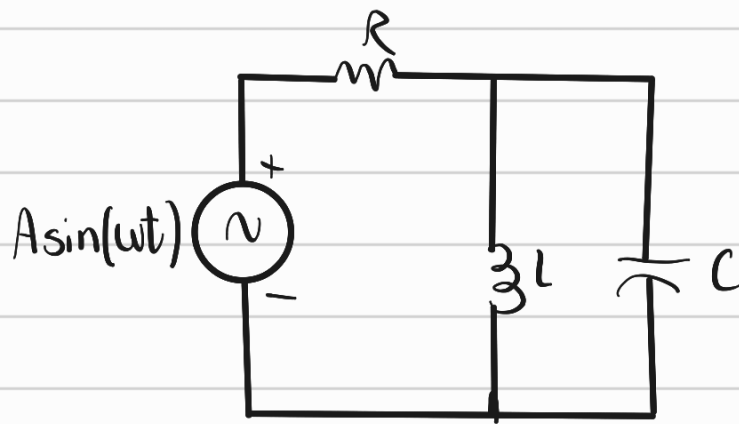


P1

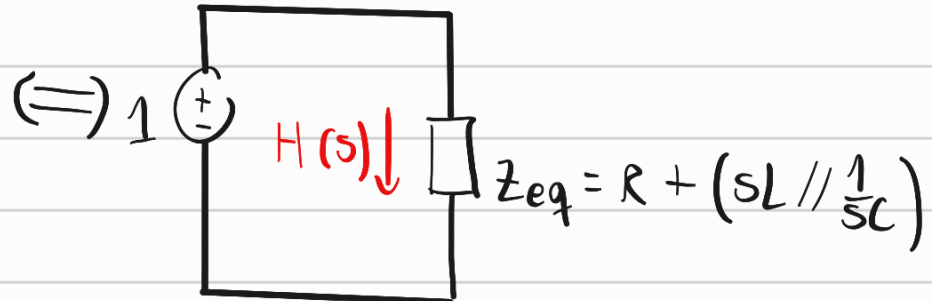

$$\begin{aligned} R &= 4 [\Omega] & 10^{-4} \\ L &= 0.1 [\text{mH}] & 10^{-2} \\ C &= 10 [\text{mF}] \\ A &= 5 [\text{V}] \\ f &= 50 \text{ Hz} \end{aligned}$$

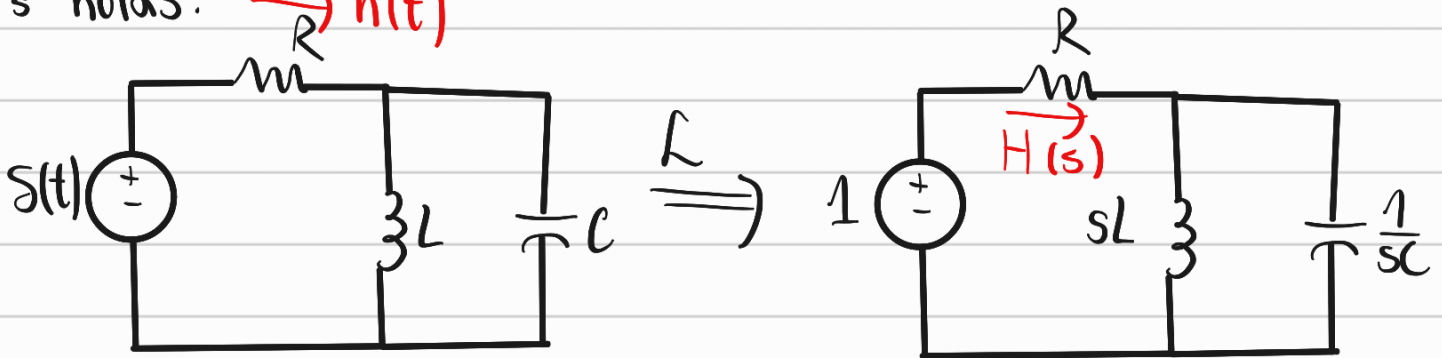a) Obtener la función de red (o respuesta al impulso, es lo mismo) Para ello consideramos la fuente como un impulso $\delta(t)$ y CI's nulas: $\rightarrow h(t)$



Por lo tanto $H(s)$ se calcula como:

$$\begin{aligned} H(s) &= \frac{1}{Z_{eq}} \\ &= \frac{1}{R + (sL // \frac{1}{sC})} \\ &= \frac{1}{R + \frac{L/c}{sL + 1/sC}} \\ &= \frac{1}{R + \frac{sL}{s^2LC + 1}} \\ &= \frac{1}{R + \cancel{sL} / (s^2LC + 1)} \end{aligned}$$

$$= \frac{C(s^2 + 1/LC)}{RC(s^2 + 1/LC) + s}$$

$$= \frac{(s^2 + 1/LC)}{R(s^2 + \frac{1}{RC}s + \frac{1}{LC})}$$

b) Queremos calcular la componente transiente de la $RESC(t)$
 Para ello calculamos la TL de la entrada y multiplicamos por $H(s)$:

$$I(s) = \mathcal{L}[5\sin(\omega t)] = 5 \int_0^\infty \sin(\omega t) e^{-st} dt$$

$$= 5 \int_0^\infty \frac{(e^{j\omega t} - e^{-j\omega t})}{2j} e^{-st} dt$$

$$= \frac{5}{2j} \left(\int_0^\infty e^{-(s-j\omega)t} dt - \int_0^\infty e^{-(s+j\omega)t} dt \right)$$

$$= \frac{5}{2j} \left[\frac{1}{s-j\omega} - \frac{1}{s+j\omega} \right]$$

(acá en la pauta anterior puse mal los signos)

otra forma conocida que para este caso no usaremos

$$\frac{5}{2j} \frac{s+j\omega - s+j\omega}{s^2 + \omega^2} = \frac{5}{2j} \frac{2j\omega}{s^2 + \omega^2} = 5 \frac{\omega}{s^2 + \omega^2}$$

Y ahora si:

$$RESC(s) = H(s) \cdot I(s)$$

$$= \frac{(s^2 + 1/LC)}{R(s^2 + \frac{s}{RC} + \frac{1}{LC})} \cdot \frac{5}{2j} \left[\frac{1}{s-j\omega} - \frac{1}{s+j\omega} \right]$$

$$= \frac{5}{2jR} \left[\frac{1}{s-j\omega} \frac{s^2 + 1/LC}{s^2 + \frac{1}{RC}s + \frac{1}{LC}} - \frac{1}{s+j\omega} \frac{s^2 + 1/LC}{s^2 + \frac{1}{RC}s + \frac{1}{LC}} \right]$$

fracciones parciales

Primero factoricemos $s^2 + \frac{1}{RC}s + \frac{1}{LC}$ encontrando sus ceros:

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

$$\Rightarrow s_{1,2} = -\frac{1}{2RC} \pm \frac{1}{2} \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}$$

(499,92187...) ≈ 1000

$$= -\frac{1}{2 \cdot 4 \cdot 10^{-2}} \left[\frac{1}{5} \right] \pm \frac{1}{2} \sqrt{\left(\frac{1}{4 \cdot 10^{-2}}\right)^2 - \frac{4}{10^{-4} \cdot 10^{-2}}} \left[\frac{1}{5} \right]$$

$$s_1 = -12.5 + 1000j = 1000.078 \angle 1.58^\circ$$

$$s_2 = -12.5 - 1000j = 1000.078 \angle -1.58^\circ$$

Por lo que de forma general, la descomposición en fracciones parciales se hace de la sgte forma:

$$\frac{s^2 + 1/LC}{(s-j\omega)(s-s_1)(s-s_2)} = \frac{a_1}{s-s_1} + \frac{a_2}{s-s_2} + \frac{a_3}{s-j\omega}$$

$$\frac{s^2 + 1/LC}{(s+j\omega)(s-s_2)(s-s_3)} = \frac{b_1}{s-s_1} + \frac{b_2}{s-s_2} + \frac{b_3}{s+j\omega}$$

$$a_1 - b_1$$

respuesta
transiente

RPS (regimen
permanente sinusoidal)

Para encontrar estos coefs descomponemos en fracciones parciales o hallando el residuo asociado a su polo respectivo, esto es:

$$a_i = \lim_{s \rightarrow s_i} (s-s_i) \frac{s^2 + \frac{1}{LC}}{(s-j\omega)(s-s_1)(s-s_2)}$$

$$b_i = \lim_{s \rightarrow s_i} (s-s_i) \frac{1}{(s+j\omega)(s-s_1)(s-s_2)}$$

Explicitamente:

$$a_1 = \lim_{s \rightarrow s_1} \frac{s^2 + \frac{1}{LC}}{(s-j\omega)(s-s_2)} = \frac{s_1^2 + \frac{1}{LC}}{(s_1-j\omega)(s_1-s_2)}$$

$$\approx \frac{25000 \angle -1.56^\circ}{1.37 \cdot 10^6 \angle -3.12^\circ}$$

$$a_2 = \lim_{s \rightarrow s_2} \frac{s^2 + \frac{1}{LC}}{(s-j\omega)(s-s_1)} = \frac{s_2^2 + \frac{1}{LC}}{(s_2-j\omega)(s_2-s_1)}$$

$$= \frac{25000 \angle 1.56^\circ}{2.62 \cdot 10^6 \angle 3.13^\circ}$$

$$b_1 = \lim_{s \rightarrow s_1} \frac{s^2 + \frac{1}{LC}}{(s+j\omega)(s-s_2)} = \frac{s_1^2 + \frac{1}{LC}}{(s_1+j\omega)(s_1-s_2)}$$

$$\approx \frac{25000 \angle -1.56^\circ}{2.62 \cdot 10^6 \angle -3.13^\circ}$$

$$b_2 = \lim_{s \rightarrow s_2} \frac{s^2 + \frac{1}{LC}}{(s+j\omega)(s-s_1)} = \frac{s_2^2 + \frac{1}{LC}}{(s_2+j\omega)(s_2-s_1)}$$

$$= \frac{25000 \angle 1.56^\circ}{1.37 \cdot 10^6 \angle 3.12^\circ}$$

Quedando: ^{transiente}

$$R_{ESC}(s) = \frac{5}{R} \frac{1}{2j} \left(\frac{(a_1 - b_1)}{(s - s_1)} + \frac{(a_2 - b_2)}{(s - s_2)} \right)$$

$\mathcal{L}^{-1} \left(\right)$

$$R_{ESC}(t) = \frac{5}{R} \frac{1}{2j} \left(e^{s_1 t} (a_1 - b_1) + e^{s_2 t} (a_2 - b_2) \right)$$

$$= \frac{5}{R} \frac{1}{2j} e^{-12.5t} \left[e^{1000jt} (a_1 - b_1) + e^{-1000jt} (a_2 - b_2) \right]$$

Definiendo $A = \frac{25000}{1.37 \cdot 10^6} \Rightarrow$

$a_1 = A \angle 1.56^\circ, b_1 = \frac{A}{2} \angle 1.56^\circ$
 $a_2 = \frac{A}{2} \angle -1.56^\circ, b_2 = A \angle -1.56^\circ$

$$R_{ESC}(t) = \frac{5}{R} \frac{1}{2j} e^{-12.5t} \left[e^{10^3 jt} \left(\underbrace{a_1 - b_1}_{= \frac{A}{2} \angle 1.56^\circ} + e^{-10^3 jt} \left(\underbrace{a_2 - b_2}_{= -\frac{A}{2} \angle -1.56^\circ} \right) \right] \right.$$

$$= \frac{5}{R} \cdot \frac{A}{2} e^{-12.5t} \frac{1}{2j} \left[e^{(10^3 t + 1.56^\circ)j} - e^{-(10^3 t + 1.56^\circ)j} \right]$$

$$= \frac{5}{R} \cdot \frac{A}{2} e^{-12.5t} \sin''(10^3 t + 1.56^\circ)$$

c) La parte transitoria desaparece para $t \gg 5 \cdot \underbrace{(2RC)}_{\tau = \frac{1}{12.5}} = 10 \cdot 4 \cdot 10^{-2} \text{ (s)}$
 $= 4 \cdot 10^{-1} \text{ [s]}$