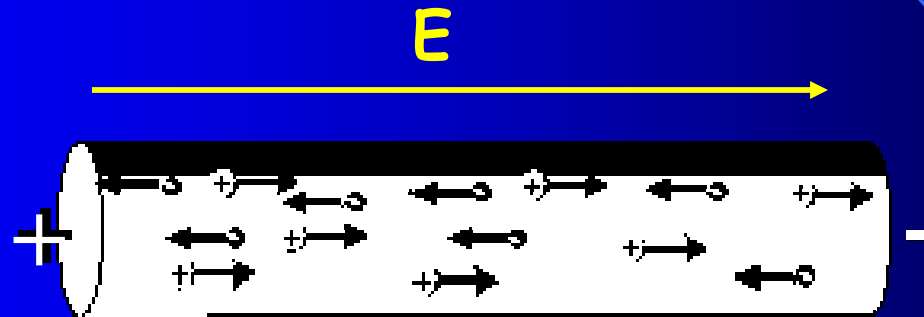


Electrodinámica

En un conductor sometido a un campo eléctrico, se observa un movimiento de cargas libres en la superficie del conductor. Por razones convencionales se ha establecido como corriente eléctrica al flujo de cargas positivas por unidad de tiempo.



$$I = \Delta q / \Delta t$$

$$I = n e v A$$

n = N° portadores de carga

e = carga del electrón

v = velocidad promedio



A = área sección transversal

$$I_{av} = \frac{\Delta Q}{\Delta t}$$

$$I = \frac{dQ}{dt}$$


En SI la unidad de corriente es el Ampere
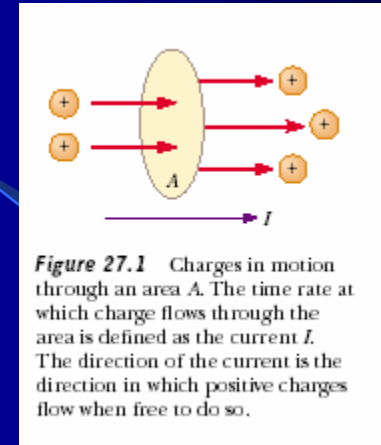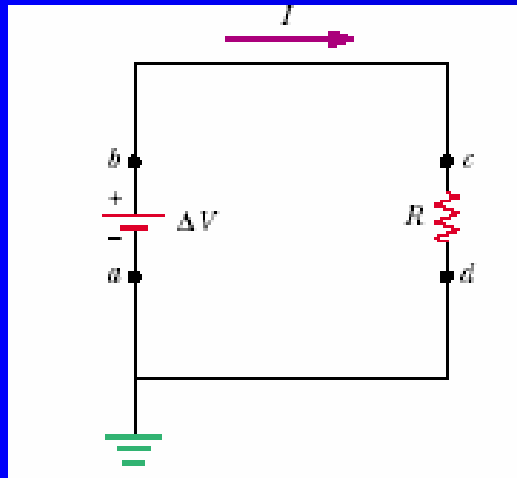
$$1 \text{ A} = \frac{1 \text{ C}}{1 \text{ s}}$$



Se le asigna ala corriente la misma direcci3n del flujo de cargas positivas


LEY de OHM

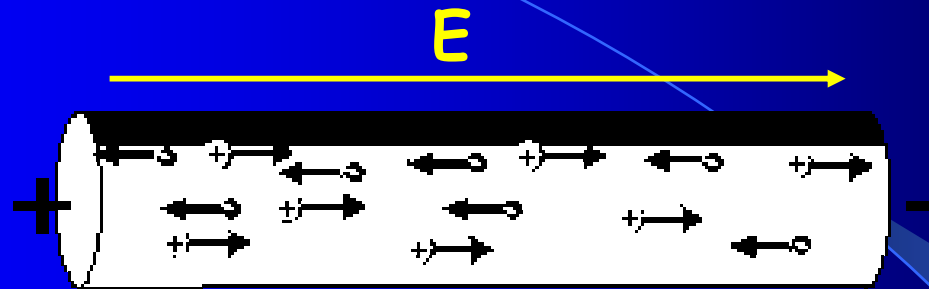

$$\left. \begin{array}{l} I \propto \Delta V \\ I \propto 1/R \end{array} \right\} I = \frac{\Delta V}{R}$$

$$I = \Delta q / \Delta t$$
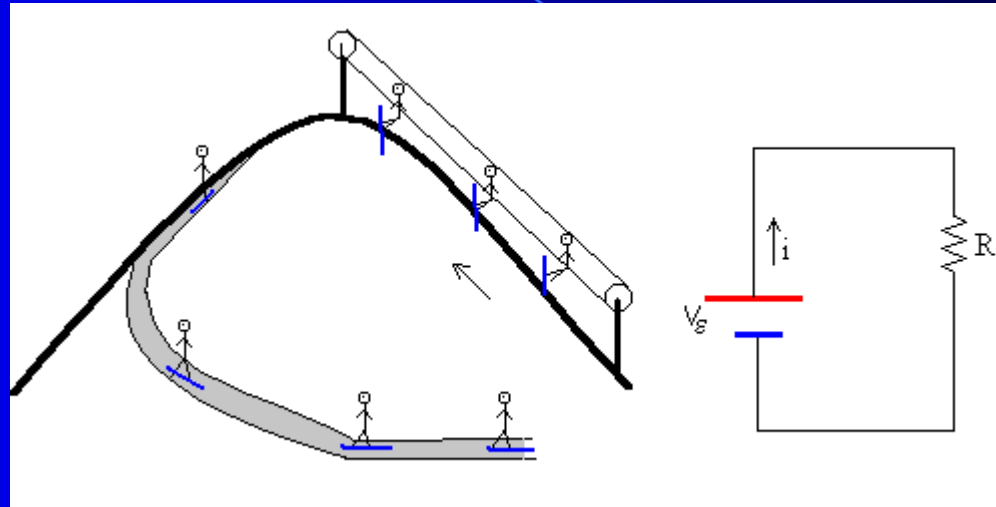
$$\text{Flujo} = \frac{\text{Volumen}}{\text{tiempo}}$$




$$I = \frac{\Delta q}{\Delta t}$$


Conductores Ohmicos

$$I = \frac{V}{R}$$

$$V = I R$$

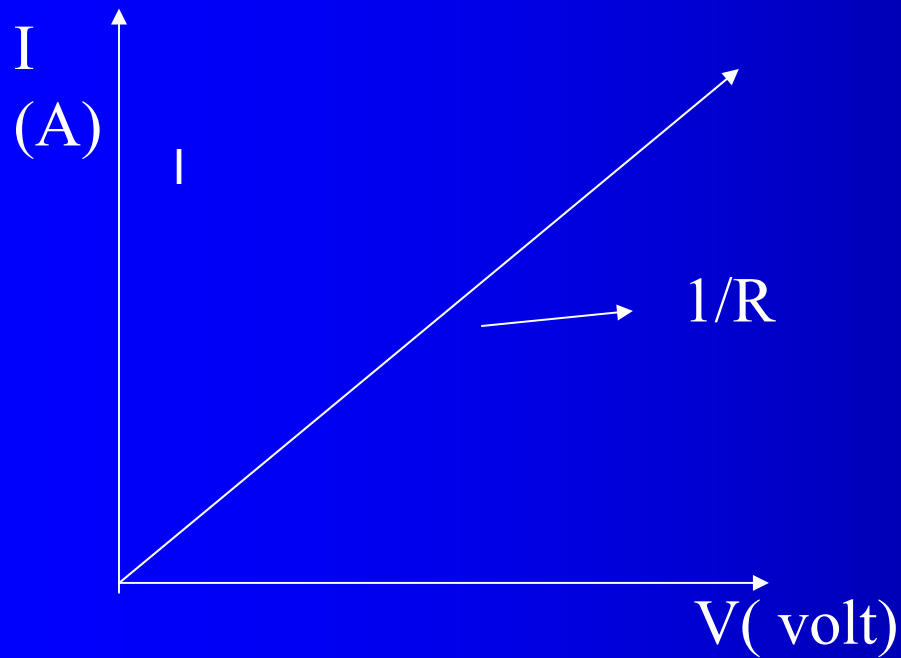

$$1/R = G$$

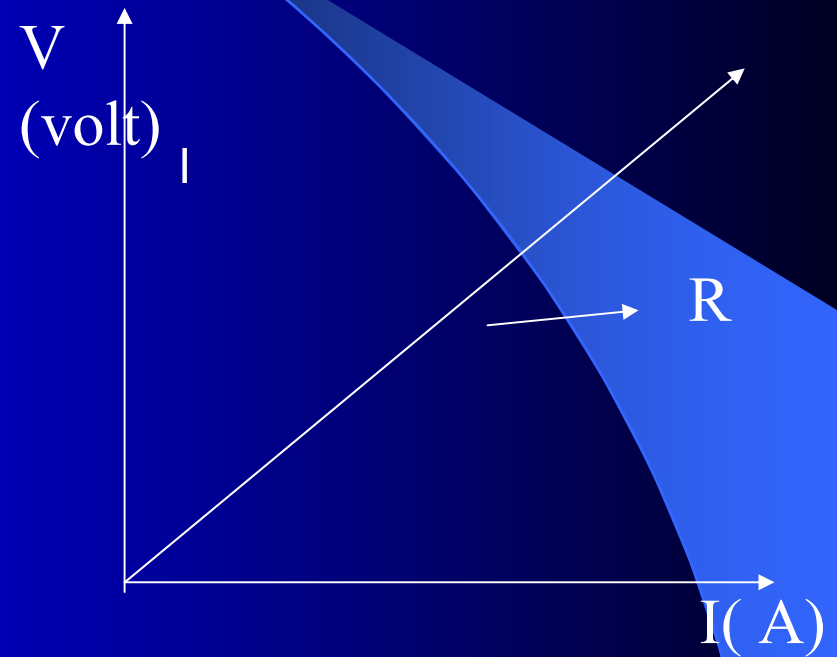

RESISTENCIA ELÉCTRICA

Cu 

$$R \propto l$$

Cu 

Cu 

$$R \propto 1/A$$

Cu 

$$R = \frac{\rho l}{A}$$

Cu 

$$R \propto \rho$$

Al 

$$R = \frac{\rho l}{A}$$

^^^

Ohm [Ω]

ρ = resistividad


l = largo

A = área sección transversal


$$G = \frac{1}{R}$$

G = conductancia

Siemens

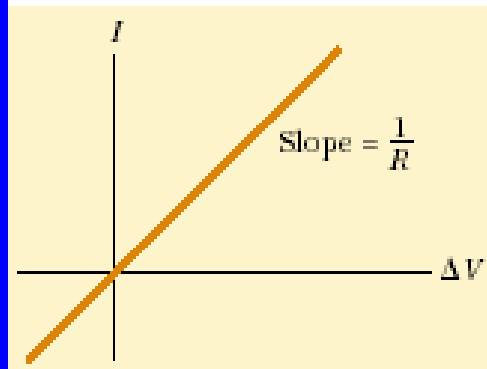

(a)

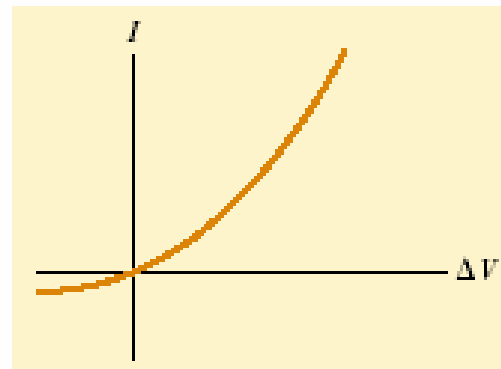

(b)

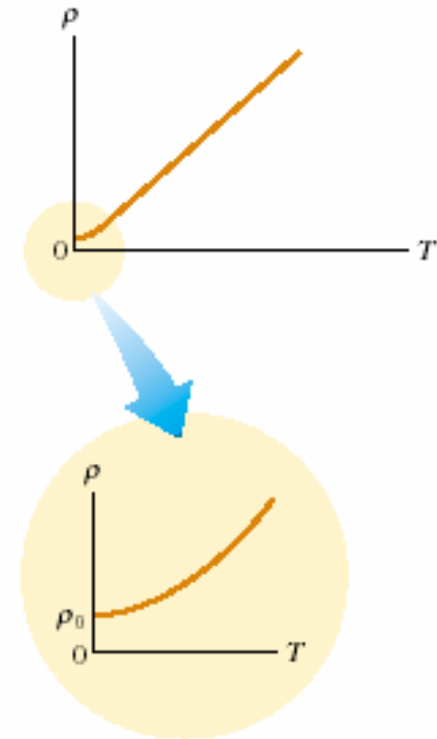


Figure 27.10 Resistivity versus temperature for a metal such as copper. The curve is linear over a wide range of temperatures, and ρ increases with increasing temperature. As T approaches absolute zero (inset), the resistivity approaches a finite value ρ_0 .

TABLE 27.2 Color Coding for Resistors

Color	Number	Multiplier	Tolerance
Black	0	1	
Brown	1	10^1	
Red	2	10^2	
Orange	3	10^3	
Yellow	4	10^4	
Green	5	10^5	
Blue	6	10^6	
Violet	7	10^7	
Gray	8	10^8	
White	9	10^9	
Gold		10^{-1}	5%
Silver		10^{-2}	10%
Colorless			20%



Amarillo rojo naranja

$$42 \times 10^3 \Omega = 42 K \Omega$$




TABLE 27.1 Resistivities and Temperature Coefficients of Resistivity for Various Materials

Material	Resistivity ^a ($\Omega \cdot \text{m}$)	Temperature Coefficient $\alpha[(^{\circ}\text{C})^{-1}]$
Silver	1.59×10^{-8}	3.8×10^{-3}
Copper	1.7×10^{-8}	3.9×10^{-3}
Gold	2.44×10^{-8}	3.4×10^{-3}
Aluminum	2.82×10^{-8}	3.9×10^{-3}
Tungsten	5.6×10^{-8}	4.5×10^{-3}
Iron	10×10^{-8}	5.0×10^{-3}
Platinum	11×10^{-8}	3.92×10^{-3}
Lead	22×10^{-8}	3.9×10^{-3}
Nichrome ^b	1.50×10^{-6}	0.4×10^{-3}
Carbon	3.5×10^{-5}	-0.5×10^{-3}
Germanium	0.46	-48×10^{-3}
Silicon	640	-75×10^{-3}
Glass	10^{10} to 10^{14}	
Hard rubber	$\approx 10^{13}$	
Sulfur	10^{15}	
Quartz (fused)	75×10^{16}	



^a All values at 20°C.^b A nickel–chromium alloy commonly used in heating elements.

CIRCUITO ELÉCTRICO

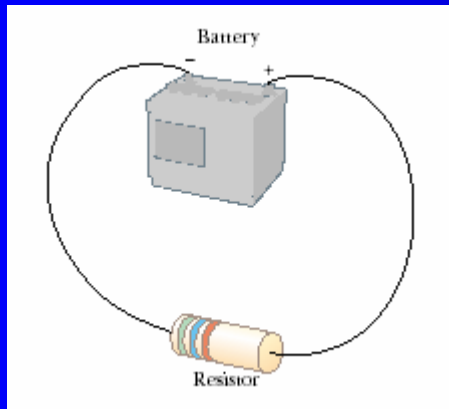fem fuente de energía (pila ,batería , red domiciliaria)




$$\mathcal{E} = \Delta V$$

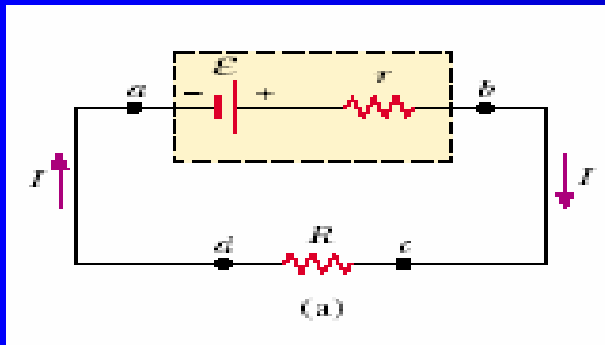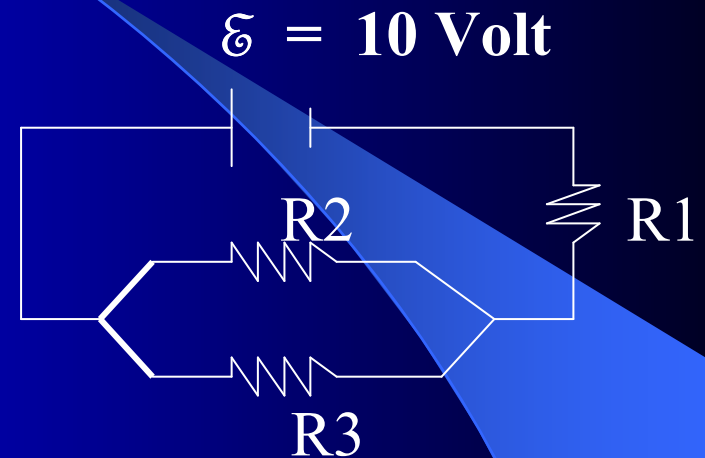


$$\Delta V = \mathcal{E} - Ir$$


Circuito R en serie

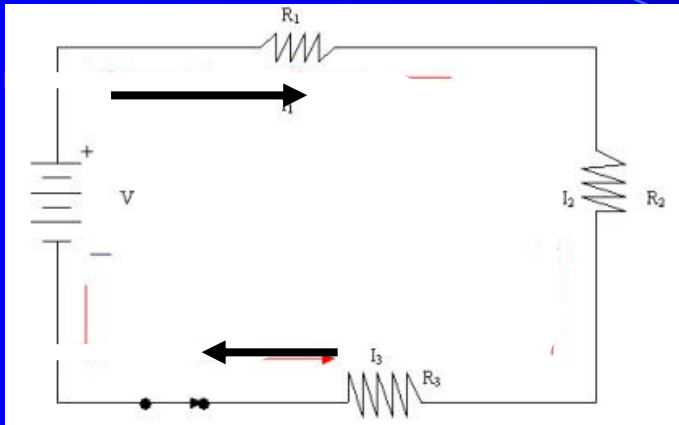

Circuito R en paralelo

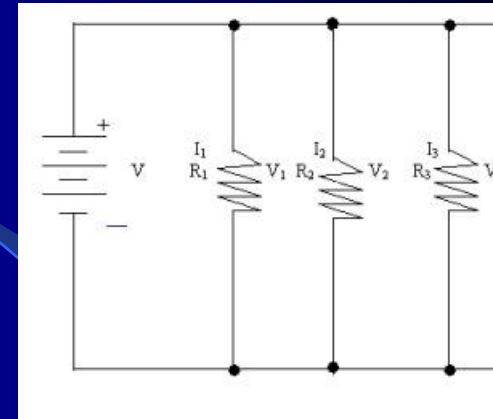

$$\Delta V = 10 \text{ Volt}$$

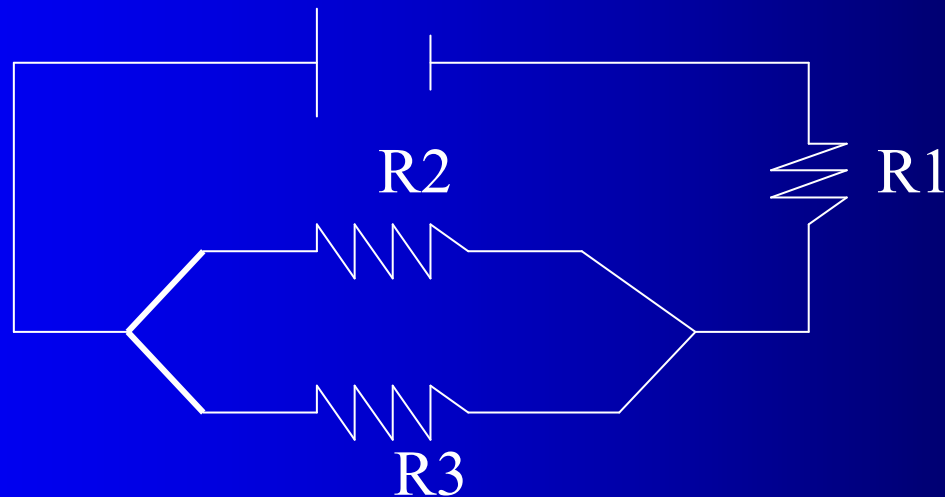



Gustav Kirchhoff (1824–1887)

1^{era} Ley Teorema de la trayectoria

♣ La suma de las diferencias de de potenciales a traves de todos los elementos del circuito en un circuito cerrado debe ser cero

$$\sum_{\text{closed loop}} \Delta V = 0$$

$$\sum \mathcal{E} = \sum IR$$


$$\sum \mathcal{E} - \sum IR = 0$$

2^{da} Ley de los nodos

♣ La suma de las corrientes que entran a un nodo es igual a la suma de las corrientes que salen del nodo

$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

$$I_1 = I_2 + I_3$$

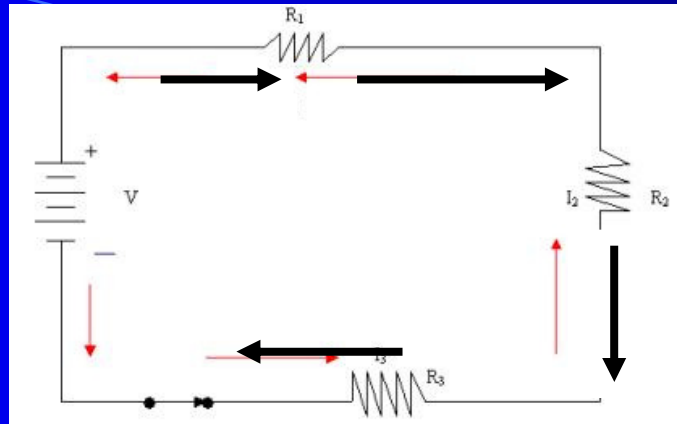


$$V = I R$$

$$I_{\text{total}} = I_1 = I_2 = I_3$$


$$V_{\text{total}} = V_1 + V_2 + V_3$$

$$I R_{\text{total}} = I_1 R_1 + I_2 R_2 + I_3 R_3 \quad / \quad I$$


$$R_{\text{total}} = R_1 + R_2 + R_3$$

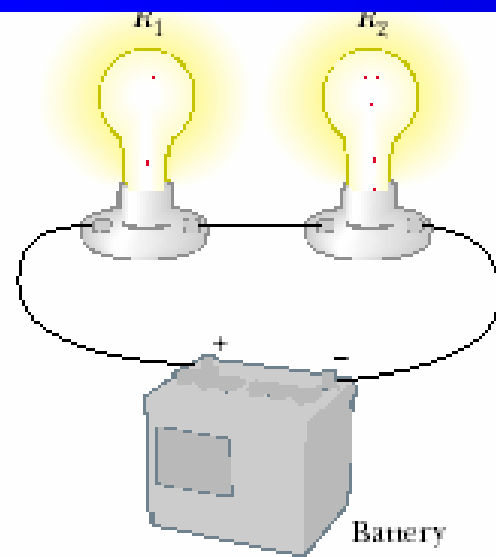


(a)

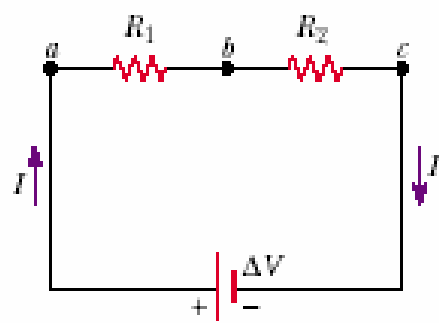

(b)

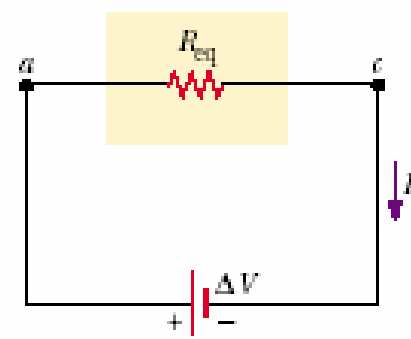

(c)

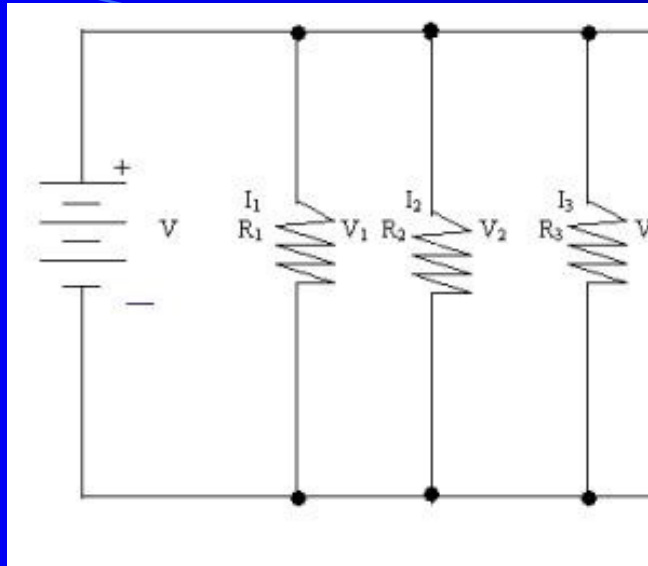

$$I = V / R$$

$$V_{\text{total}} = V_1 = V_2 = V_3$$

$$I_{\text{total}} = I_1 + I_2 + I_3$$

$$\frac{V_{\text{total}}}{R_{\text{total}}} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \quad \bigg/ \quad V$$

$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

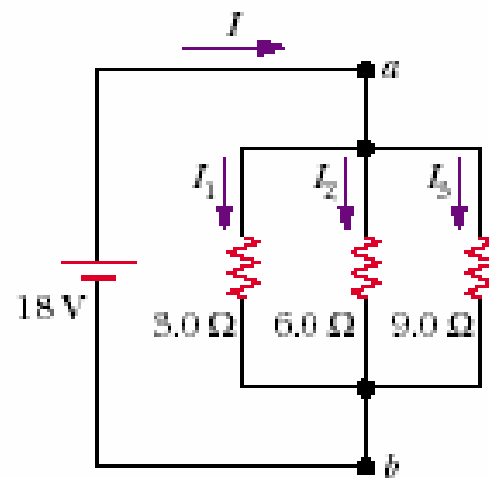


Figure 28.7 Three resistors connected in parallel. The voltage across each resistor is 18 V.


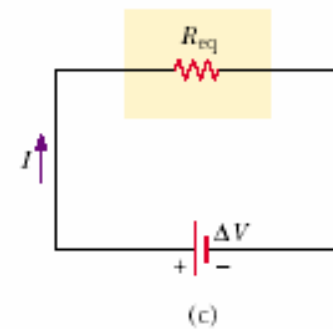
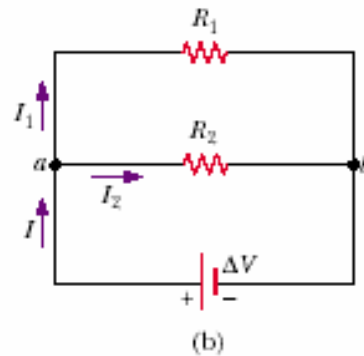
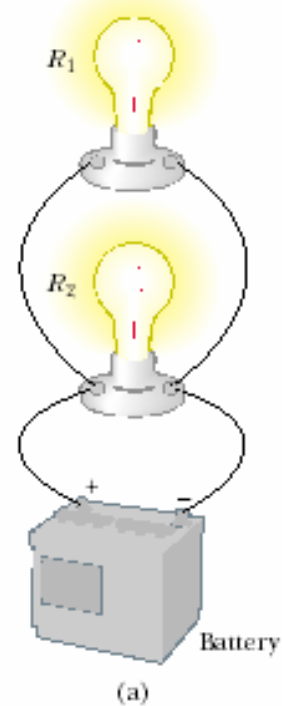


Figure 28.5 (a) A parallel connection of two resistors R_1 and R_2 . The potential difference across R_1 is the same as that across R_2 . (b) Circuit diagram for the two-resistor circuit. (c) The resistors replaced with a single resistor having an equivalent resistance $R_{\text{eq}} = (R_1^{-1} + R_2^{-1})^{-1}$.

paralelo

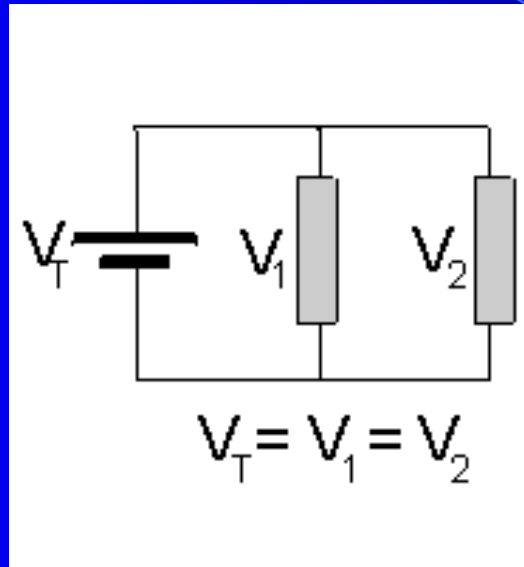

En el caso de conexión en paralelo la diferencia de potencial es la misma.


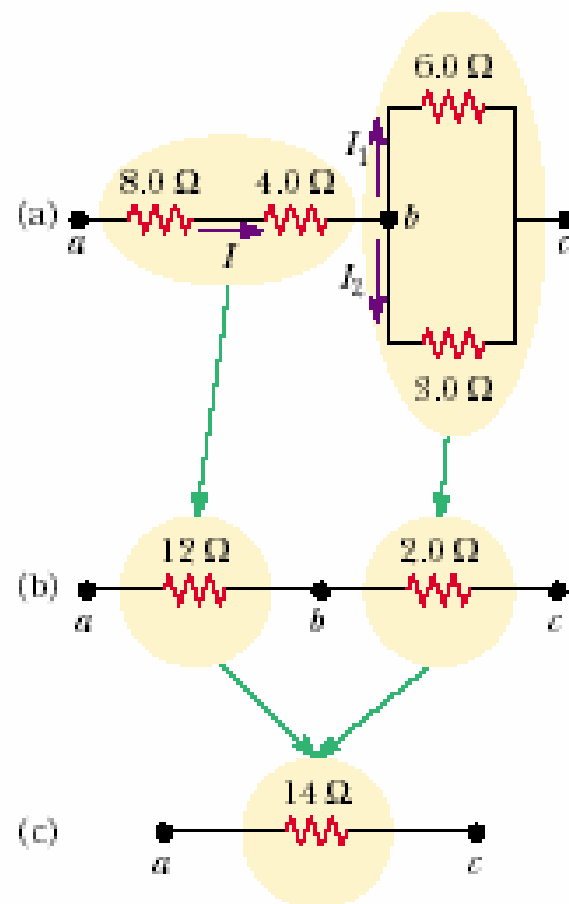


Figure 28.6

Resistencias en paralelo

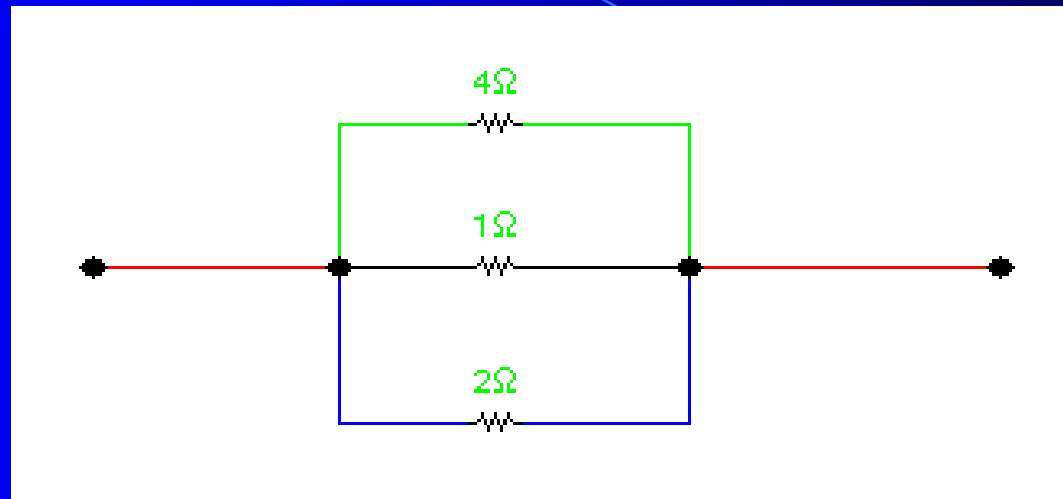

$$\frac{1}{R_t} = \frac{1}{4} + \frac{1}{1} + \frac{1}{2} \left(\frac{1}{\Omega} \right)$$


$$\frac{1}{R_t} = \frac{1+4+2}{4}$$

$$R_t = 4/7 \Omega$$

$$R_t = 0,57 \Omega$$

¿Cuál es la resistencia total del circuito?
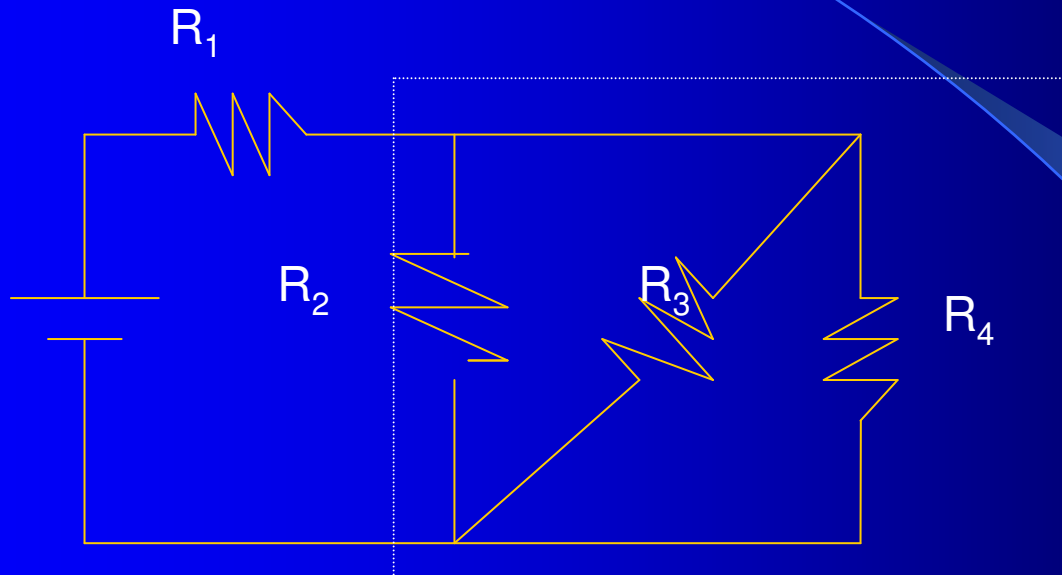
$$R_1 = 100 \, \Omega, \quad R_2 = 50 \, \Omega, \quad R_3 = 25 \, \Omega, \quad R_4 = 75 \, \Omega$$




$$\frac{1}{R_e} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$= \frac{1}{50} + \frac{1}{25} + \frac{1}{75} \quad \frac{1}{R_e} = \frac{3+6+2}{150}$$

$$R_e = \frac{150}{11} \longrightarrow 13,63 \, \Omega$$

$$R_t = 100 + 13,63 = 113,63 \, \Omega$$

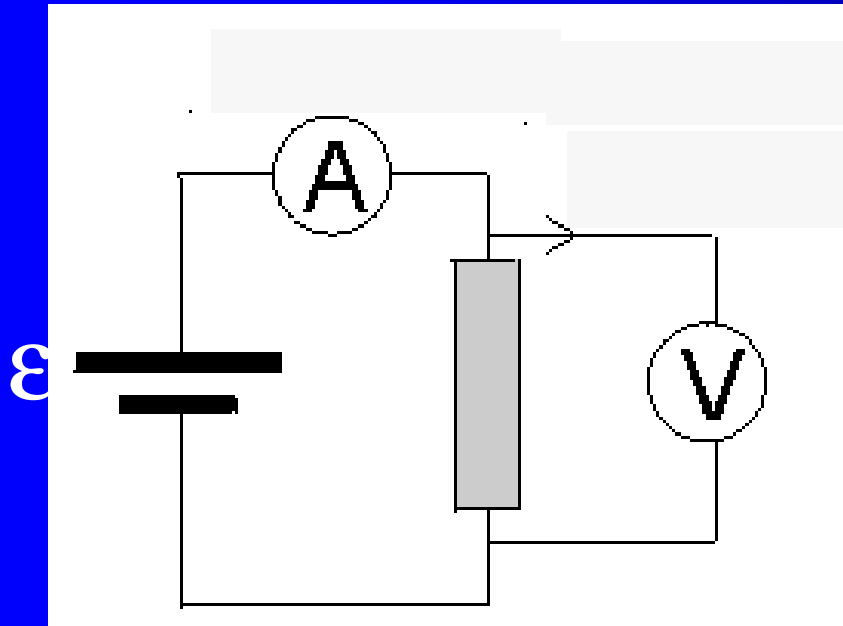

A: **amperímetro**,
se conecta en serie.

V: **voltímetro** se conecta
en paralelo

I = corriente en amperes (coulomb/seg)
 V = voltaje en volts (joules/coulomb)

Energía Eléctrica y Potencia

$$\Delta U = q \Delta V$$

La rapidez de pérdida de energía en la resistencia

$$\frac{\Delta U}{\Delta t} = \frac{\Delta Q}{\Delta t} \Delta V = I \Delta V$$

$$\mathcal{P} = I \Delta V$$

La unidad de potencia SI = watts

$$\mathcal{P} = I^2 R = \frac{(\Delta V)^2}{R}$$

$$I = \frac{\Delta V}{R}$$

$$\mathcal{P} = I \Delta V$$

$$\mathcal{P} = I^2 R$$



Figure 27.15 Power companies transfer electrical energy at high potential differences.

$$\mathcal{P} = I \Delta V$$

